

EEE 2243
Digital System Design
TEST 1

1. a) Write the Verilog code for the following Boolean function WITHOUT minimization using Boolean expression approach: $f = \sum m(1,3,4,5,10,12,13)$
(CO1) [10 marks]

```
1  ⇨      00012
3  ⇨      00112
4  ⇨      01002
5  ⇨      01012
10 ⇨      10102
12 ⇨      11002
13 ⇨      11012


module FuncQ1a(a, b, c, d, f1);

input a, b, c, d;
output f1;

assign f1 =    (~a & ~b & ~c & d)
               | (~a & ~b &  c & d)
               | (~a &  b & ~c & ~d)
               | (~a &  b & ~c &  d)
               | ( a & ~b &  c & ~d)
               | ( a &  b & ~c & ~d)
               | ( a &  b & ~c &  d);


endmodule
```

Simulation:

 

- b) Draw the FSM diagram for a 4-bit mod 5 counter starting at 4 and decrement by 3. Then write the Verilog code for it.

(CO1) [15 marks]

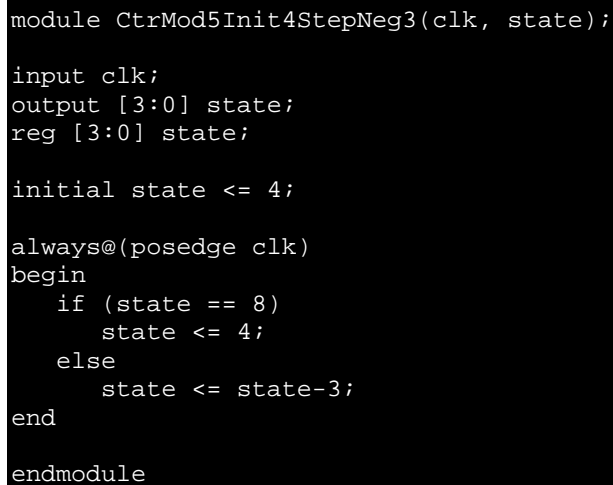

2. Figure Q2 shows the output waveform of 4-bit Johnson and ring counters. Write the Verilog code for them using BOOLEAN expression and BEHAVIORAL approach. (Four code to be written.) [Hint: Draw the logic circuit / diagram first.] (CO1) [20 marks]


 


Figure Q2

Johnson counter:

 

Boolean:

```
module JohnsonBoolean(clk, state);
```

```
input clk;
```

```
output [3:0] state;
```

```
reg [3:0] state;
```

```
initial state <= 0;
```

```
always@(posedge clk)
```

```
begin
```

```
    state[0] <= state[1];
```

```
    state[1] <= state[2];
```


```
    state[2] <= state[3];
```

```
    state[3] <= ~state[0];
```

```
end
```

```
endmodule
```

Simulation:

 

Behavioral:

```
module JohnsonBehavioral(clk, state);
```

```
input clk;
```

```
output [3:0] state;
```

```
reg [3:0] state;
```

```
initial state <= 0;
```

```
always@(posedge clk)
```

```
begin
```

```
case (state)
```

```
4'b0000: state <= 4'b1000;
```

```
4'b1000: state <= 4'b1100;
```

```
4'b1100: state <= 4'b1110;
```

```
4'b1110: state <= 4'b1111;
```

```
4'b1111: state <= 4'b0111;
```

```
4'b0111: state <= 4'b0011;
```

```
4'b0011: state <= 4'b0001;
```


```
4'b0001: state <= 4'b0000;
```

```
endcase
```


```
end
```

```
endmodule
```

Simulation:

 


Ring counter:

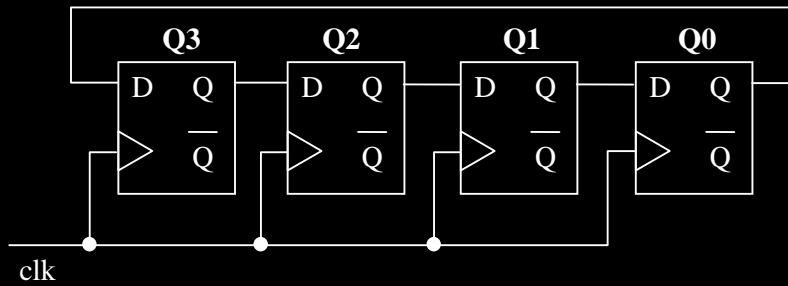

Boolean:

```
module RingBoolean(clk, state);  
  
    input clk;  
    output [3:0] state;  
    reg [3:0] state;  
  
    initial state <= 4'b1000;  
  
    always@(posedge clk)  
    begin  
        state[0] <= state[1];  
        state[1] <= state[2];  
        state[2] <= state[3];  
        state[3] <= state[0];  
    end  
  
endmodule
```


Simulation:

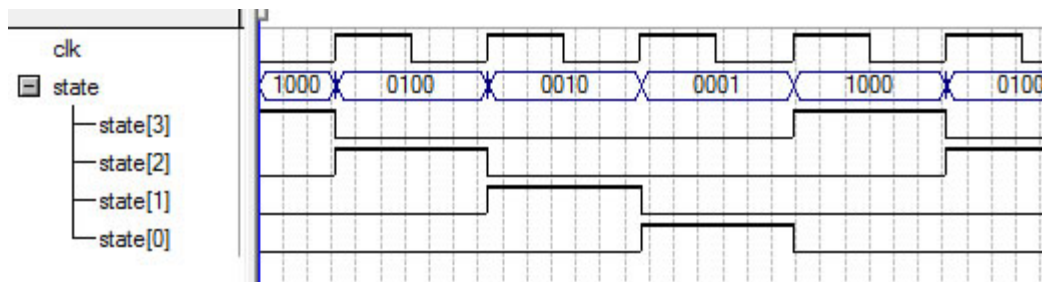

Behavioral:

```
module RingBehavioral(clk, state);  
  
input clk;  
output [3:0] state;  
reg [3:0] state;  
  
initial state <= 4'b1000;  
  
always@(posedge clk)  
begin  
    case (state)  
        4'b1000: state <= 4'b0100;  
        4'b0100: state <= 4'b0010;  
        4'b0010: state <= 4'b0001;  
        4'b0001: state <= 4'b1000;  
    endcase  
end  
  
endmodule
```


Simulation:

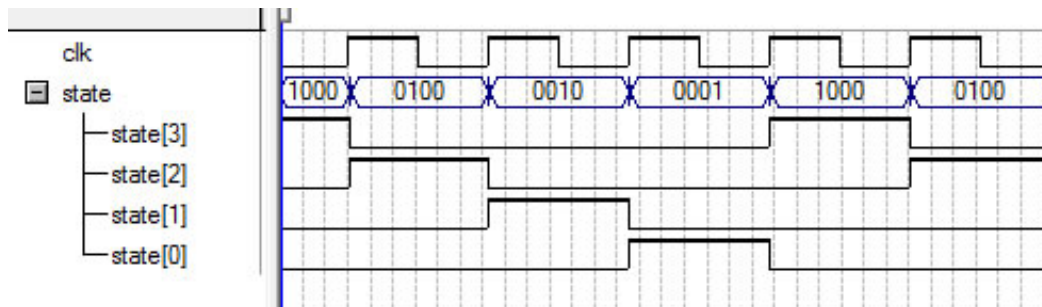


3. a) Write the Verilog code for a 2-to-4 decoder WITHOUT any enable input.
(CO1) [5 marks]

```
module Decoder_2_4(Lin, Lout);  
  
input [1:0] Lin;  
output [3:0] Lout;  
  
assign Lout[0] = ~Lin[1] & ~Lin[0];  
assign Lout[1] = ~Lin[1] & Lin[0];  
assign Lout[2] = Lin[1] & ~Lin[0];  
assign Lout[3] = Lin[1] & Lin[0];  
  
endmodule
```

Simulation:

 

RTL View:

 

- b) Re-use the code in (a) to write a code for 3-to-8 decoder with or without additional components. [Hint: You need to figure out how to put all outputs of one of the decoders to all 0-s when it is not selected.]

(CO1) [15 marks]

```
module Decoder_3_8(Lin, Lout);
    input [2:0] Lin;
    output [7:0] Lout;
    wire [7:0] w;


    Decoder_2_4 MSB(.Lin({Lin[1], Lin[0]}),
        .Lout({w[7], w[6], w[5], w[4]}));

    Decoder_2_4 LSB(.Lin({Lin[1], Lin[0]}),
        .Lout({w[3], w[2], w[1], w[0]}));


    assign Lout[0] = w[0] & ~Lin[2];
    assign Lout[1] = w[1] & ~Lin[2];
    assign Lout[2] = w[2] & ~Lin[2];
    assign Lout[3] = w[3] & ~Lin[2];
    assign Lout[4] = w[4] & Lin[2];
    assign Lout[5] = w[5] & Lin[2];
    assign Lout[6] = w[6] & Lin[2];
    assign Lout[7] = w[7] & Lin[2];

endmodule
```

Simulation:

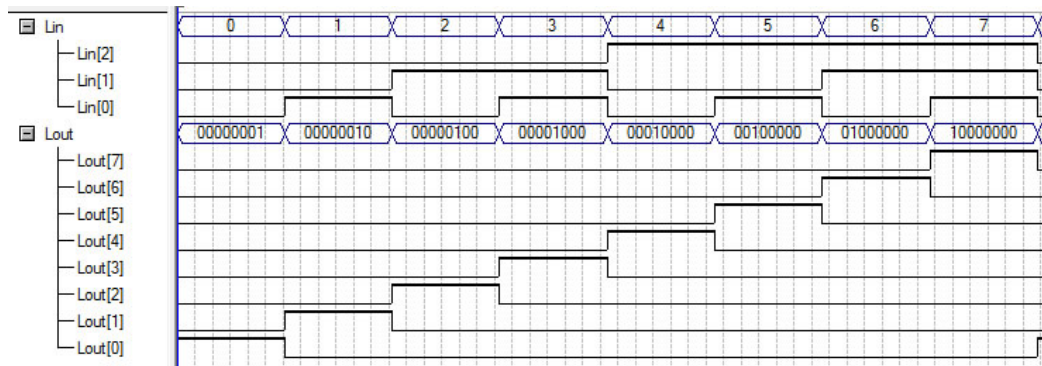

RTL View:

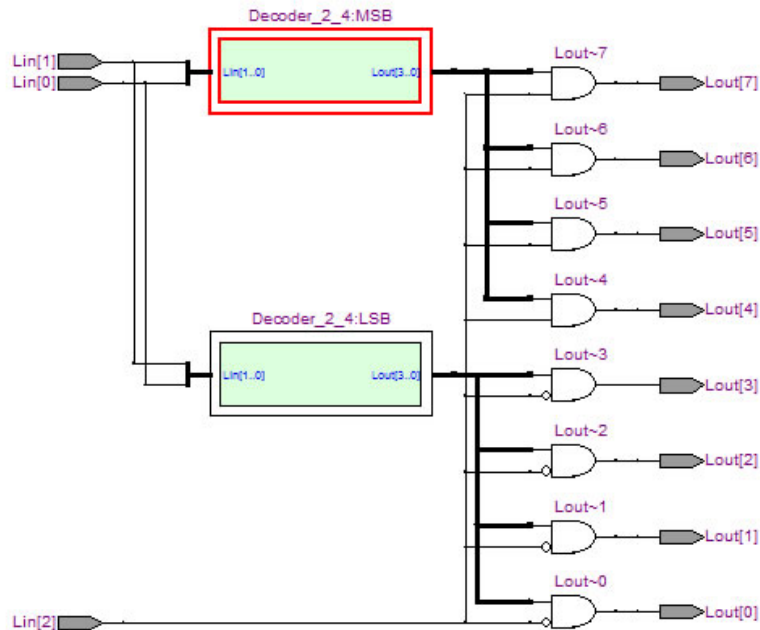

4. a) Explain the steps you use to perform bit-by-bit magnitude comparison.
(CO2) [10 marks]

Algorithm to compare A and B starting at MSB:

- If the bit are the same repeat to compare next LSB
- Else if bit A is 1 and bit B is 0 then stop by giving condition $A > B$
- Else if bit A is 0 and bit B is 1 then stop by giving condition $A < B$

- b) Figure 4(b) shows a block diagram of a single stage of a bit-by-bit magnitude comparator. Explain (with drawing) how you construct a 4-bit magnitude comparator out of it.

(CO2) [10 marks]


 


Figure Q4(b)

 4 bit comparator is constructed by cascading the 1 bit comparators lt_out to lt_in , gt_out to gt_in and eq_out to eq_in from MSB to LSB. The inputs at MSB is set as: $lt_in = 0$, $gt_in = 0$ and $eq_in = 1$. This way the comparison can propagate to the next bit. The outputs at LSB is the output of the 4 bit comparator.



- c) Based on the information you have or gave in (a) and (b), write the Verilog code for the 1-bit magnitude comparator in BEHAVIORAL mode.

(CO1) [15 marks]

```
module Comp(lt_in, gt_in, eq_in,
            lt_out, gt_out, eq_out,
            a, b);

input lt_in, gt_in, eq_in, a, b;
output lt_out, gt_out, eq_out;
reg lt_out, gt_out, eq_out;

always@(*)
begin
    if (lt_in)
    begin
        lt_out <= 1;
        gt_out <= 0;
        eq_out <= 0;
    end
    else if (gt_in)
    begin
        lt_out <= 0;
        gt_out <= 1;
        eq_out <= 0;
    end
    else if (eq_in)
    begin
        if (a == b)
        begin
            lt_out <= 0;
            gt_out <= 0;
            eq_out <= 1;
        end
    end
end
```

Simulation:

